
EC806 DSD using FPGA

LAB - 3

 

Report Submission

By
Inbasekaran Perumal
201EC226

Pranav Koundinya 201EC247

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING NATIONAL INSTITUTE OF TECHNOLOGY KARNATAKA, SURATHKAL SRINIVASNAGAR 575025 KARNATAKA INDIA

27 September 2023

1. Behavioral verilog code for (a) 2 to 4 decoder (b) M to N decoder	
Verilog code	
a) 2 to 4 decoder	
b) M to N decoder	4
Simulation results	5
a) 2 to 4 decoder	5
b) M to N decoder	5
Resource utilization	6
a) 2 to 4 decoder	6
b) M to N decoder	6
2. Verilog code to Count the number of 1s in a 8 bit number	6
Verilog code	6
Simulation results	8
Resource utilization	8
3. Verilog code to Implement F(v,w,x,y,z) = (0, 2, 3, 4, 8, 21, 22, 29, 31)	8
Verilog code	8
Simulation results	9
Resource utilization	10
4. Verilog code to model a 16 bit magnitude comparator	10
Verilog code	10
Simulation results	11
Resource utilization	11
5. Verilog code to Count the number of leading 0s in an 8 bit number	12
Verilog code	12
Simulation results	13
Resource utilization	13

1. Behavioral verilog code for (a) 2 to 4 decoder (b) M to N decoder

Verilog code


a) 2 to 4 decoder

```
module two_four_decoder(
input [1:0]w,
input En,
output reg [3:0]y
);
always @*
begin
if(~En)
y = 4'b0000;
else
y = 1 << w;
end
endmodule
`timescale 1ns/1ps
module two four decoder tb();
reg [1:0]w;
reg En;
wire [3:0]y;
integer i;
two_four_decoder dut (w, En, y);
initial
begin
for (i = 0; i < 8; i = i + 1)
begin
\{En, w\} <= i;
#50;
end
$stop;
end
endmodule
```


b) M to N decoder

```
module M N decoder(
w, En, y
);
parameter M = 4;
parameter N = 2 * *M;
input [M-1:0]w;
input En;
output reg [N-1:0]y;
always @*
begin
if(~En)
y = \{N\{1'b0\}\};
else
y = 1 << w;
end
endmodule
`timescale 1ns/1ps
module M_N_decoder_tb();
reg [3:0]w;
reg En;
wire [15:0]y;
integer i;
M N decoder dut (w, En, y);
initial
begin
for(i = 0; i < 32; i = i + 1)
begin
\{En, w\} <= i;
#50;
end
$stop;
end
endmodule
```

a) 2 to 4 decoder

 


b) M to N decoder

 


Resource utilization

a) 2 to 4 decoder

 


b) M to N decoder

 

 
2. Verilog code to Count the number of 1s in a 8 bit number

```
module ones count (
```

```
input [7:0]x,
output reg [3:0]y
);
integer i;
always @(x)
begin
y = 'b0;
for(i = 0; i < 8; i = i + 1)
y = y + x[i];
end
endmodule
`timescale 1ns/1ps
module ones_count_tb();
reg [7:0]x;
wire [3:0]y;
ones_count dut(x, y);
initial
begin
x <= 8'h69; #50
x <= 8'hff; #50
x <= 8'h00; #50
x \le 8'h4a; #50;
$stop;
end
endmodule
```




Resource utilization

 


3. Verilog code to Implement F(v,w,x,y,z) = (0, 2, 3, 4, 8, 21, 22, 29, 31)

```
module sop(input [4:0]x, output reg f); always @(*) begin
```

```
if(x == 0 || x == 2 || x == 3 || x == 4 || x == 8 || x == 21 || x == 22 ||
x == 29 \mid \mid x == 31)
f = 1;
else
f = 0;
end
endmodule
`timescale 1ns/1ps
module sop tb();
reg [4:0]x;
wire y;
integer i = 0;
sop dut (x, y);
initial
begin
for (i = 0; i < 32; i = i + 1)
begin
x \ll i;
#50;
end
//$stop;
end
Endmodule
```

 


Resource utilization

 

 4. Verilog code to model a 16 bit magnitude comparator

```
module comp 16(In1, In2, Gt, Eq, Lt);
input [15:0] In1, In2;
output Gt, Lt, Eq;
assign Gt = (In1 > In2) ? 1'b1 : 1'b0;
assign Lt = (In1 < In2) ? 1'b1 : 1'b0;
assign Eq = (In1 == In2) ? 1'b1 : 1'b0;
endmodule
`timescale 1ns/1ps
module comp 16 tb();
reg [15:0] In1, In2;
wire Gt, Lt, Eq;
comp 16 dut(In1,In2,Gt,Eq,Lt);
initial
begin
In1 = 16'b0001 1001 0001 1001;
In2 = 16'b1111 1111 0001 1001;
#50
In2 = 16'b1110 1000 0001 1001;
```

```
In1 = 16'b1110_1101_0001_1001;
#50
In1 = 16'b1110_1111_0001_1001;
In2 = 16'b1110_1111_0001_1001;
#50;
end
endmodule
```




Resource utilization



 5. Verilog code to Count the number of leading 0s in an 8 bit number

```
module leading zeros(
input [7:0]x,
output reg [3:0]y
);
always @(x)
begin
casex(x)
8'b000000000 : y = 4'b1000;
8'b00000001 : y = 4'b0111;
8'b0000001x : y = 4'b0110;
8'b000001xx : y = 4'b0101;
8'b00001xxx : y = 4'b0100;
8'b0001xxxx: y = 4'b0011;
8'b001xxxxx: y = 4'b0010;
8'b01xxxxxx: y = 4'b0001;
8'b1xxxxxxx: y = 4'b0000;
endcase
end
endmodule
`timescale 1ns/1ps
module leading_zeros_tb();
reg [7:0]x;
wire [3:0]y;
leading zeros dut (x, y);
initial
begin
x = 8'b0010 1010; #50
x = 8'b1110 0111; #50
x = 8'b1111 11111; #50
x = 8'b1111_0110; #50;
end
endmodule
```



Resource utilization

